

## The exponential diode

A theoretical analysis of the  $p$ - $n$  junction structure yields a single equation which describes the forward-bias and reverse-bias operation:

$$i_A = I_S \left( \exp \frac{v_A}{n \cdot V_T} - 1 \right)$$

$I_S$  is the reverse saturation current (in the range of  $\mu\text{A}$  for germanium and  $\text{pA}$  for silicon). A better name is the “scale current”; it arises from the fact that  $I_S$  is directly proportional to the cross-sectional area of the diode (e.g. – for a double area device we get a double value of diode current  $i_A$  for the same diode voltage  $v_A$ ).

$V_T$  is the thermal voltage;  $V_T = \frac{k \cdot T}{q}$  with a typical value:  $V_T = 26 \text{ mV}$  for  $T = 300 \text{ K} = 27 \text{ degr.C}$ .

- $k$  is the Boltzmann constant ( $= 1.38 \cdot 10^{-23} \text{ J/K}$ ),
- $T$  is the absolute temperature (in Kelvin).
- $q$  is the electronic charge ( $= 1.6 \cdot 10^{-19} \text{ C}$ ).

$n = 1 \dots 2$  is a coefficient; diodes made using the standard integrated circuits fabrication process exhibits  $n = 1$  (when operated in normal conditions) while diodes available as discrete two-terminal devices generally exhibits  $n = 2$ .

## Forward bias – voltage-current relationship

For  $v_A \gg V_T$ , the exponential factor is much greater than unity, hence the “1” can be neglected in the diode equations and:

$$i_A = I_S \exp \frac{v_A}{n \cdot V_T}.$$

The exponential relationship between diode current and diode voltage means that:

- the forward current is much larger than the reverse current and
- the forward current increase very rapidly with small increases in  $v_A$ .

To derive a different relationship, sometimes more useful, one can consider two currents

for two corresponding voltages:  $i_1 = I_S \exp \frac{v_1}{n \cdot V_T}$ ,  $i_2 = I_S \exp \frac{v_2}{n \cdot V_T}$ . The current ratio is:

$$\frac{i_1}{i_2} = \exp \frac{v_1 - v_2}{n \cdot V_T}, \text{ which can be rewritten as: } v_1 - v_2 = n \cdot V_T \ln \frac{i_1}{i_2} = 2.3 \cdot n \cdot V_T \lg \frac{i_1}{i_2}.$$


This equation simply states that for a decade (factor of 10) change in current, the diode voltage drop changes by “ $2.3 \cdot n \cdot V_T$ ”, which is about 60 mV for  $n = 1$  and 115 mV for  $n = 2$ .

A convenient approximate number of 0.1 V / decade for the slope of the diode logarithmic characteristic can be used (if the coefficient  $n$  is not known).

A small silicon rectifier diode can be considered to have a 0.6 V voltage drop at a current  $i_A = 1 \text{ mA}$  and a 0.1 V voltage drop change for a decade change in current.

## Temperature dependence

At a given constant diode current, the voltage drop across the diode decreases by approximately 2 mV for every degree Celsius increase in temperature.

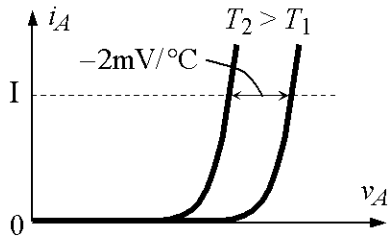

**Figure** The temperature influence over the forward characteristics of the diode;

At a constant current, the voltage drop decreases by about 2mV for every degree Celsius increase in temperature.

## The *pn* Junction in the Breakdown Regime

The two possible breakdown mechanisms are the Zener effect (with a breakdown voltage  $V_Z < 5$  V) and the avalanche effect (that occurs when  $V_Z$  is greater than about 7 V).


In heavily doped junctions, the depletion layer is very narrow and the electrical field becomes so strong that it can dislocate electrons directly from the covalent bonds and generate electron-hole pairs. These electrons and holes produce a rapid increase in reverse current (once the reverse blocking voltage is exceeded). This is the Zener breakdown process.

The avalanche breakdown occurs at a certain value of the electrical field, when the minority carriers gain sufficient kinetic energy to be able to break covalent bonds in atoms with which they collide. These new liberated carriers may themselves produce still more mobile electrons and holes through additional collisions; a rapid build-up of reverse current results (with a negligible change in the voltage drop across the junction).

The *pn* junction breakdown is not a destructive process, provided that the maximum specified power dissipation is not exceeded. Special diodes, called Zener diodes, have been manufactured to operate in the breakdown regime of the *pn* junction.
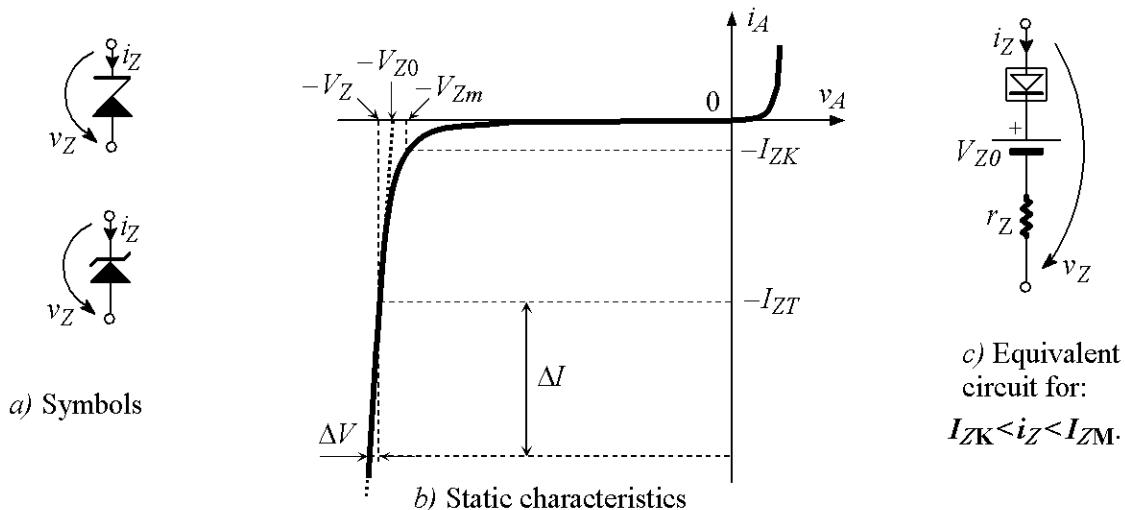
## Zener Diodes

In normal applications of Zener diodes, current flows into the cathode and the cathode is positive with respect to the anode:  $i_Z = -i_A > 0$ ,  $v_Z = -v_A > 0$ .



The Zener diode maintains an essentially constant voltage across its terminals over a specific range in reverse current values. A minimum value of reverse current  $I_{ZK}$  (knee current) must be maintained in order to keep diode in regulation. There is a maximum

current  $I_{ZM}$ , above which the diode may be damaged (the maximum permitted power  $P_{dZM} = V_Z I_{ZM}$ , is exceeded).

## Zener Equivalent Circuits

The ideal approximation: the voltage drop across the Zener diode is constant  $v_Z = V_Z$  for a positive Zener current  $i_Z > 0$ ; the diode model is an ideal diode in series with a constant voltage source  $V_Z$ .

A more complex model indicated in the previous figure includes a series resistance; that is the incremental resistance of the Zener diode and it represents the ratio of voltage to

current change:  $r_Z = \frac{\Delta v_Z}{\Delta i_Z}$ . The Zener data-sheet indicates the Zener voltage and  $r_Z$  at a

particular value of current  $I_{ZT}$ , called the Zener test current.

Another parameter of the diode is the temperature coefficient that specifies the percent change in Zener voltage for each degree C change in temperature. A Zener diode with a nominal breakdown voltage of 5.1 V exhibits a point of zero temperature coefficient at modest current levels.


Forward biased, a Zener diode acts as a normal rectifier diode.

## Zener Applications
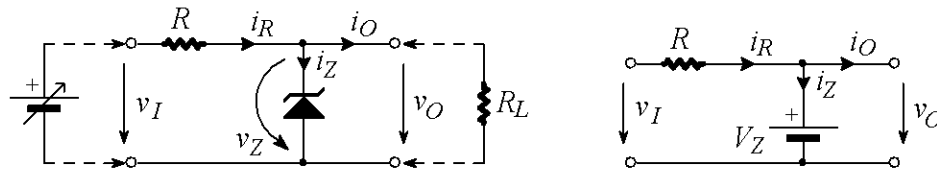
### The Voltage Regulator

A voltage regulator is a circuit whose purpose is to provide a constant dc voltage in spite of changes in the load current and possible changes in the dc power supply that feeds the regulator circuit.

The circuit of figure is known as a "shunt regulator" because the Zener diode is connected in parallel (shunt) with the load.



The changes in the load current and the input voltage variations are transformed by the circuit in zener current variations. If we consider the ideal Zener model, for:  $I_{ZK} < i_Z < I_{ZM}$ ,  $v_Z = V_Z$  and  $v_O = v_Z = V_Z = \text{ct}$ .

The limits of  $v_I$  and  $i_O$  for the circuit to work correctly can be found with the ideal Zener model.

To analyze the influence of input voltage, the output current will be considered constant:

$$i_O = \text{ct} = I_O, \quad i_Z = i_R - i_O = \frac{v_I - V_Z}{R} - i_O > I_{ZK} \quad \text{and} \quad v_I > V_Z + R \cdot (I_{ZK} + I_O). \quad \text{In any case } v_I > V_Z.$$

$$\text{For } v_I = \text{ct} = V_I, \quad i_O < \frac{v_I - V_Z}{R} - I_{ZK}.$$

When the output terminals are open, the load current is zero, all the current is through the Zener and the current in the resistor is constant (for a given input voltage):  $i_r = \frac{v_I - V_Z}{R}$ .

When a load resistance is connected part of this current is through the Zener and part of it through the load:  $i_R = i_Z + i_O$ . As  $R_L$  decreases,  $i_O$  goes up and  $i_Z$  goes down. The circuit continues to regulate until  $i_Z$  reach its minimum value  $I_{ZK}$ . At this point the load current reaches its maximum value (with the regulator working properly).

Two parameters can be used to measure how well the regulator is performing its function:

- The Line Regulation:  $LineRg = \left. \frac{\Delta v_O}{\Delta v_I} \right|_{I_O = ct}$  – it represents the change in  $v_O$  corresponding to a 1 V change in  $v_I$ .
- The Load Regulation:  $LoadRg = \left. \frac{\Delta v_O}{\Delta i_O} \right|_{V_I = ct}$  – it represents the change in  $v_O$  corresponding to a 1 mA change in  $i_O$ .

### The Maximum Limiting Resistance

The Zener current should be at least equal to the knee current in any conditions supported by the regulator; that means:  $i_{Zmin} > I_{ZK}$ . The worst case for  $i_{Zmin}$

$$i_{Zmin} = \frac{v_{I\_min} - V_Z}{R} - i_{Omax} > I_{ZK} \text{ gives the limiting resistance: } R \leq \frac{v_{I\_min} - V_Z}{i_{Omax} + I_{ZK}}.$$

### Applications:

**S4 – P1.** Design a voltage regulator supplied by  $v_I = 9 \dots 12$  V for a maximum output current  $i_{OM} = 100$  mA. Consider an ideal zener diode with  $V_Z = 5.1$  V ( $i_{ZK} = 0$  and  $r_Z = 0$ ).

Determine the series resistor value, maximum power dissipated by the resistor and by the zener diode.

$$R \leq \frac{v_{I\_min} - V_Z}{i_{Omax} + I_{ZK}} = \frac{9 - 5.1}{100m} = 39 \Omega, \quad P_{dRM} = \frac{(v_{I\_max} - V_Z)^2}{R} = \frac{(12 - 5.1)^2}{39} = \frac{47.6}{39} = 1.22 \text{ W},$$

$$P_{dZM} = V_Z \cdot i_{Zmax} = V_Z \frac{v_{I\_max} - V_Z}{R} = 5.1 \frac{12 - 5.1}{39} = 5.1 \cdot 0.177 = 0.9 \text{ W}.$$

**S4 – P2.** It is required to design a zener shunt regulator to provide a regulated voltage of about 10 V. The available 10-V 1W zener of type 1N4740 is specified to have a 10 V drop at a test current of 25 mA. At this current its typical  $r_Z$  is  $7 \Omega$ . The raw supply available has a nominal value of 20 V but can vary as much as  $\pm 25\%$ . The regulator is required to supply a load current of 0 to 80 mA, Design for a minimum zener current of 5 mA.


- a) Find  $V_{Z0}$ .
- b) Calculate the required value of  $R$ .
- c) What is the change in  $V_O$  expressed as a percentage, corresponding to the  $\pm 25\%$  change in  $V_S$ ?
- d) By what percentage does  $V_O$  change from the no-load to the full-load condition?

- e) What is the maximum current that the zener in your design should be able to conduct? What is the zener power dissipation under these condition?

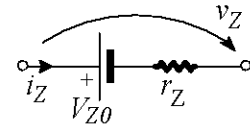- a) From the zener equivalent circuit:  $v_Z = V_{Z0} + r_Z i_Z$ ;

At  $I_{ZT}$  we get  $V_{ZT} = V_{Z0} + r_Z I_{ZT}$  and

$$V_{Z0} = V_{ZT} - r_Z I_{ZT} = 10 - 7 \cdot 25m = 9.825V.$$




- b) The main condition for the circuit to work correctly is  $i_Z > I_{ZK}$ , for any  $i_Z$  that can appear in the circuit;  $i_Z = i_R - i_O = \frac{v_S - V_Z}{R} - i_O$ .

The previous inequality applied for minimum  $i_Z$  can be

used to compute  $R$ ,  $i_{Z\min} = \frac{v_{S\min} - V_Z}{R} - i_{O\max} > I_{ZK}$  and

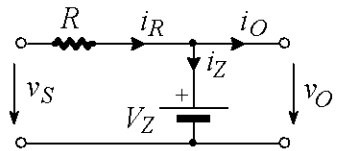
$$R \leq \frac{v_{S\min} - V_Z}{i_{O\max} - I_{ZK}} = \frac{0.75 \cdot 20 - 10}{20m + 5m} = \frac{5}{25m} = 200\Omega.$$



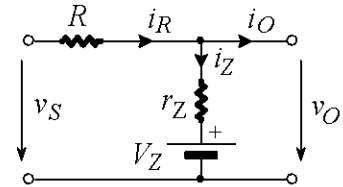- c) Line regulation for  $i_O = 0$  ( $i_R = i_Z$ ):  $v_O = V_{Z0} + r_Z i_Z$ ,

$$v_O = V_{Z0} + r_Z \frac{v_S - V_{Z0}}{R + r_Z}; \Delta v_O = r_Z \frac{\Delta v_S}{R + r_Z} = 7 \frac{10}{207} = 0.338V.$$

$$LineRg = \frac{\Delta v_O}{\Delta v_I} \cdot 100 = \frac{0.338}{10} \cdot 100 = 3.38\% \text{ (34 mV/V)}.$$



- d) Assume the nominal value of raw supply:  $V_S = 20V$ .

$$\text{For no-load condition we get: } v_{O\max} = V_{Z0} + r_Z \frac{V_S - V_{Z0}}{R + r_Z} = 9.825 + 7 \frac{20 - 9.825}{207} = 10.169V.$$

For full-load condition, the zener current is minimum and the output voltage is minimum:

$$i_Z \left(1 + \frac{r_Z}{R}\right) = \frac{V_S - V_{Z0}}{R} - i_O, \quad i_{Z\min} = \frac{\frac{V_S - V_{Z0}}{R} - i_{O\max}}{1 + \frac{r_Z}{R}} = \frac{\frac{20 - 9.825}{200} - 20m}{1 + \frac{7}{200}} = \frac{30.875}{1.035} = 29.83mA.$$

$$v_{O\min} = V_{Z0} + r_Z i_{Z\min} = 9.825 + 7 \cdot 29.83m = 10.034V; \text{ LoadRg} = \frac{\Delta v_O}{\Delta i_O} = \frac{10.169 - 10.034}{20m} = 6.75\Omega.$$

That is also the Thevenin equiv.resistance seen at the output:  $R_T = r_Z \parallel R = \frac{7 \cdot 200}{207} = 6.76\Omega$ .

- e) The maximum zener current (and voltage) appears for the no-load condition:

$$i_{Z\max} = \frac{V_{S\max} - V_{Z0}}{R + r_Z} = \frac{25 - 9.825}{207} = 73.3mA, \quad v_{Z\max} = V_{Z0} + r_Z i_{Z\max} = 9.825 + 7 \cdot 73m = 10.34V.$$

The maximum power dissipated by zener is:  $P_{dZ\max} = v_{Z\max} \cdot i_{Z\max} = 10.34 \cdot 73m \cong 0.76W$ .

#### S4 – P3.

- a) Determine the parameter of a zener diode ( $V_Z$  and  $r_Z$ ) if one measured  $v_{Z1} = 6.3V$  at  $i_{Z1} = 50mA$  and  $v_{Z1} = 6.3V$  at  $i_{Z2} = 100mA$ .
- b) Utilizing this diode, design a voltage regulator supplied by  $v_I = 12 \dots 15V$  for an output current  $i_O = 20 \dots 80mA$ . Consider  $i_{ZK} = 5mA$ . (Determine  $R$  and  $P_{dRM}$ .)
- c) Determine the output voltage limits ( $v_{O\min}$  and  $v_{O\max}$ ).